



# **Chapter 3**

# **Current Electricity**

# Chapter 3

## Current Electricity

BOARD-2013

1. Write the corresponding values of  $x$  and  $y$  for which the lengths of conductors  $x = 4\Omega$  and  $y = 48 \times 10^{-8} \Omega \cdot \text{m}$  are reduced to half. (1)

$$\Rightarrow x = 4\Omega$$


↳ Resistance ( $R \propto l$ )  
So when length reduces to half -  
 $x = 2\Omega$

$$y = 48 \times 10^{-8} \Omega \cdot \text{m}$$

↳ Resistivity ( $\rho$  doesn't depend on length)  
So,  $y = 48 \times 10^{-8} \Omega \cdot \text{m}$

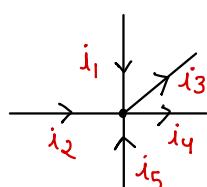2. Write Kirchhoff's first rule (Law of junction). Drawing a circuit diagram of wheatstone bridge, derive condition for zero deflection in the bridge.

$\Rightarrow$  **Kirchhoff's Junction Rule** - At any junction, the sum of the currents entering the junction is equal to the sum of currents leaving the junction.




$$i_1 + i_2 + i_5 = i_3 + i_4$$

↳ Incoming      Outgoing

→ Applicable for both loop and Open type cir.  
→ Conservation of charge.

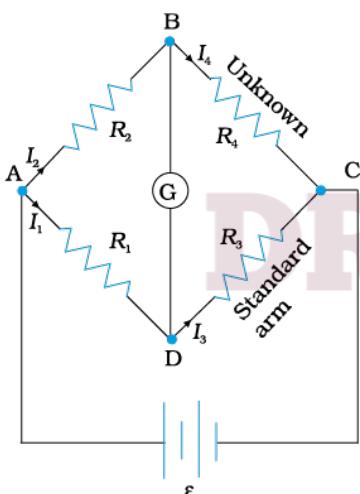**wheatstone bridge** - Suppose there are four resistors  $R_1, R_2, R_3, R_4$  connected in w.B. Battery is connected b/w A & C and Galvanometer connected b/w B & D.



→ In balanced conditions resistor are such that there are no current through Galvanometer.

→ By Kirchhoff's junction rule on junction B & D -

$$I_1 = I_3$$

$$I_2 = I_4$$

→ By Kirchhoff's loop rule in ADDA -

$$-I_1 R_1 + I_2 G + I_2 R_2 = 0$$

$$-I_1 R_1 + I_2 R_2 = 0 \quad \{ I_2 G = 0 \}$$

$$I_1 R_1 = I_2 R_2 \quad \text{---} \textcircled{1}$$

in loop CDAB -

$$-I_3 R_3 + I_2 G + I_4 R_4 = 0$$

$$-I_3 R_3 + I_2 R_4 = 0$$

$$I_3 R_3 = I_2 R_4 \quad \text{---} \textcircled{2}$$

$$\text{Eq}^n \textcircled{1} \div \text{Eq}^n \textcircled{2}$$

$$\frac{I_1 R_1}{I_1 R_3} = \frac{I_2 R_2}{I_2 R_4}$$


$$\frac{R_1}{R_3} = \frac{R_2}{R_4}$$

Note - If  $R_1, R_2, R_3$  are known resistor and  $R_4$  are unknown resistor then

$$R_4 = \frac{R_2 R_3}{R_1}$$

3. In the given circuit write the value of resultant resistance in b/w  $x$  and  $y$  when Key  $K$  is -

(i) open      (ii) closed

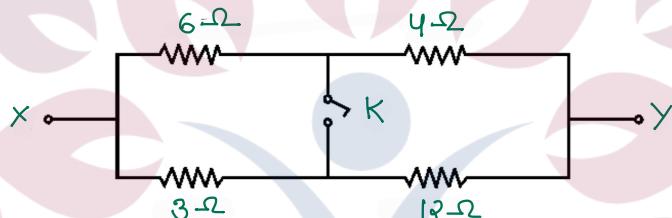

1. when Key is open:-  $R_1 = 6\Omega$  &  $R_2 = 4\Omega$  are in series

$R_3 = 3\Omega$  &  $R_4 = 12\Omega$  are in series

$$R_{12} = R_1 + R_2 = 6 + 4 = 10\Omega$$

$$R_{34} = R_3 + R_4 = 3 + 12 = 15\Omega$$

→ Now  $R_{12}$  &  $R_{34}$  are in parallel.

$$\frac{1}{R} = \frac{1}{R_{12}} + \frac{1}{R_{34}}$$

$$\frac{1}{R} = \frac{1}{10} + \frac{1}{15} = \frac{3+2}{30}$$

$$R = \frac{30}{5} = 6\Omega$$

2. when Key is close -  $R_1$  &  $R_3$  are in parallel  
&  $R_2$  &  $R_4$  are in parallel

$$\frac{1}{R_{13}} = \frac{1}{R_1} + \frac{1}{R_3}$$

$$\frac{1}{R_{13}} = \frac{1}{6} + \frac{1}{3} = \frac{1+2}{6}$$

$$R_{13} = 2\Omega$$

$$\frac{1}{R_{24}} = \frac{1}{R_2} + \frac{1}{R_4}$$

$$\frac{1}{R_{24}} = \frac{1}{4} + \frac{1}{12} = \frac{3+1}{12}$$

$$R_{24} = 3\Omega$$

$$R = R_{13} + R_{24}$$

$$R = 2 + 3 = 5\Omega$$

## BOARD-2013 (Supp.)

4. Write unit and dimension of mobility of charge. (1 Marks)


$$\Rightarrow \mu = \frac{Vd}{E}$$

(Drift velocity per unit electric field)

$$\text{unit} - \frac{m/s}{V/m} = m^2/Vs$$

$$\text{Dimension} - [M^{-1}L^0T^2A^1]$$

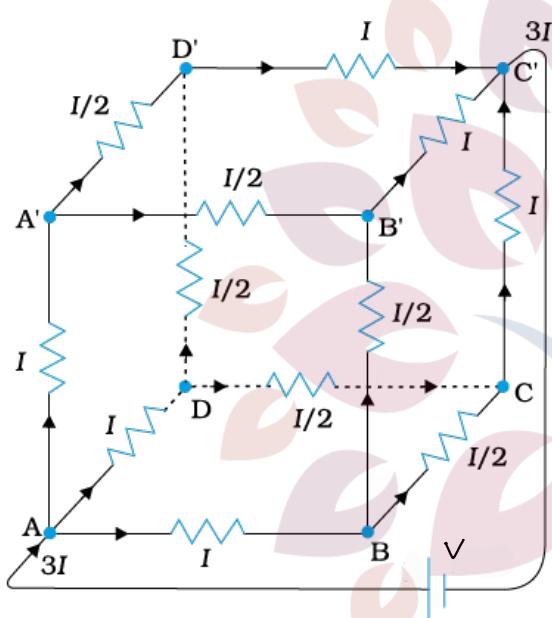5. If resistance each of  $\sigma$ - $\Omega$  resistance are joined in cubical network, then calculate the equivalent resistance  $R$  at the corner opposite to diagonals of this network.



- This network is not reducible to a simple series and parallel combination of resistors.
- So, we use symmetric arrangement to obtain eq. resistance.
- Apply Kirchoff's Second Rule b/w A & C' point -

$$-I\sigma - \frac{I\sigma}{2} - I\sigma + V = 0$$

$$V = I\sigma + \frac{I\sigma}{2} + I\sigma$$

By Ohm's Law

$$3IR = I(\sigma + \frac{\sigma}{2} + \sigma)$$

$$3R = \frac{2\sigma + \sigma + 2\sigma}{2}$$

$$R = \frac{5\sigma}{6} \Omega$$

## BOARD-2014

6. Obtain equation of  $\vec{J} = \sigma \vec{E}$  (2 Marks)

(basis of drift velocity)

Ans-  $J$  (current density) -

$$J = \frac{I}{A} \quad \text{--- (1)}$$

Relation b/w  $I$  &  $V_d$  (drift velocity)

$$I = nA V_d e$$

put in eq<sup>n</sup> (1)

$$J = \frac{nA V_d e}{A}$$

$$J = n V_d e \quad \text{--- (2)}$$

By definition of drift velocity -

$$V_d = \frac{eE}{m} \tau$$

where  $e = e^-$   
 $E = \text{Electric field}$   
 $m = \text{mass}$   
 $T = \text{Relaxation time}$

$$J = ne \left( \frac{eE}{m} \right) T$$

$$J = \frac{n e^2 T}{m} E$$


$$\sigma = \frac{n e^2 T}{m}$$

↳ conductivity

$$J = \sigma E$$

7. Two cells of emf  $E_1$  &  $E_2$  are connected in series. Their internal resistance are  $r_1$  &  $r_2$ . Compute eq. resistance & eq. emf.

Ans.

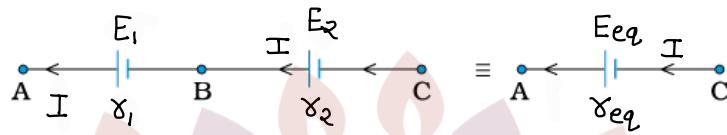

combination of cells in which one terminal of a cell is joined with opposite terminal of 2<sup>nd</sup> cell, is known as series combination.

→ Suppose two cells of  $E_1$  &  $E_2$  emf and  $r_1$  &  $r_2$  internal resistance. Current flowing in both are same but terminal voltage on both cell is different i.e.  $V_1$  &  $V_2$ .

$$V = V_1 + V_2$$

$$V = E_1 - I r_1 + E_2 - I r_2$$

$$V = (E_1 + E_2) - I (r_1 + r_2)$$

→ If we wish to replace the combination by a single cell b/w A & C of emf  $E_{eq}$  and  $r_{eq}$  internal resistance we would have -

$$V = E_{eq} - I (r_{eq})$$

→ Compare both -

$$E_{eq} = E_1 + E_2$$

$$r_{eq} = r_1 + r_2$$

→ Current (I)  $\Rightarrow$

$$I = \frac{\text{E.M.F.}}{\text{Total resistance}}$$

$$I = \frac{E_{eq}}{R + r_{eq}}$$

$$I = \frac{E_1 + E_2}{R + r_1 + r_2}$$

→ if n cell -

$$E_{eq} = E_1 + E_2 + \dots$$

$$r_{eq} = r_1 + r_2 + \dots$$

$$I = \frac{E_{eq}}{R + r_{eq}}$$

→ if n cell of same emf and internal resistance -

$$E_{eq} = nE$$


$$r_{eq} = n\sigma$$

$$I = \frac{nE}{R + n\sigma}$$

$$I = \frac{E}{R + \sigma/n}$$

## BOARD-2015

8. Find Ratio of resistivity-

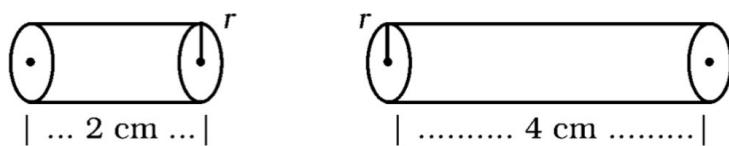


⇒  $\rho_1/\rho_2 = 1$  both have same resistivity because, resistivity only depends on nature and

9. Find value of  $I$  - [1]



## BOARD-2016

10. Determine Resistance - [1]

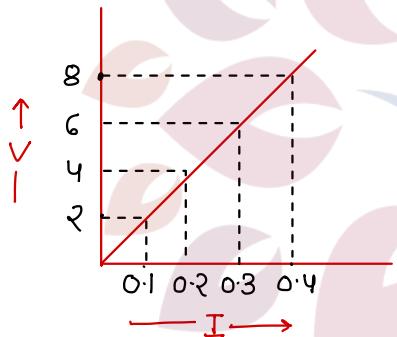

$$R = \frac{\Delta V}{\Delta I} = \frac{8-2}{0.4-0.1}$$


$$R = \frac{6}{0.3} = 20\Omega$$

11. Write the unit of current density. [1]

⇒ Current flowing perpendicular to unit area of cross-section is called current density.

$$\vec{J} = \frac{\vec{I}}{A} \quad \text{Unit: } A/m^2$$

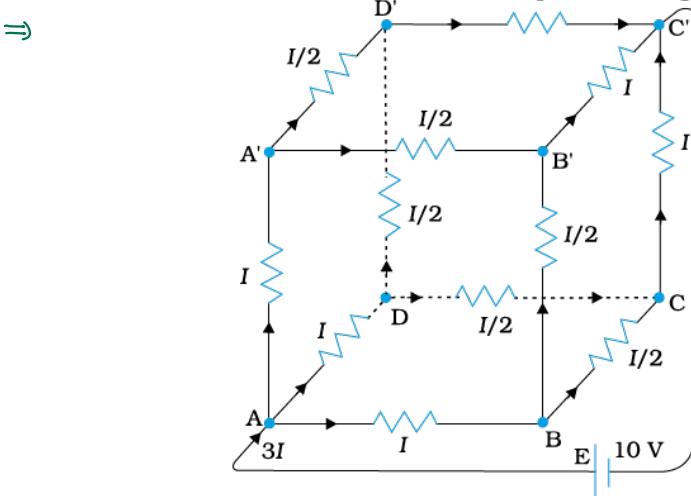12. Write Kirchoff's first rule. A battery of 10V and negligible internal resistance is connected to diagonally opposite corner of cubic network consisting of 12 resistors each of  $1\Omega$ . Determine eq. resistance. [3 Marks]



→ This network is not reducible to a simple series and parallel combination of resistors.  
→ So, we use symmetric arrangement to obtain eq. resistance.  
→ Apply Kirchoff's Second Rule b/w A & C' point -  
 $-I\delta - \frac{I\delta}{2} - I\delta + V = 0$

$$V = I\delta + \frac{I\delta}{2} + I\delta$$

$$(3I)R = I \left( \frac{R}{2} + \frac{R}{2} + R \right)$$

$$3R = \frac{2R + R + 2R}{2}$$

$$R = \frac{5R}{6} = \frac{5}{6} \times 12 = 10\ \Omega$$


### BOARD-2017

13. Define drift velocity of electrons in a conductor. [1]  
 ⇒ Average velocity of  $e^-$  in opposite direction of electric field is called Drift velocity.

$$\vec{V}_d = -\frac{e\vec{E}}{m}t \quad \text{unit: m/s}$$

14. What is Ohm's Law? Write its two limitation. [2 Marks]  
 ⇒ If physical condition such as length of conductor, cross-section area, temperature, nature of material remain constant then potential difference across the conductor will be directly proportional to the electric current flowing in the conductor.

#### Limitation:-

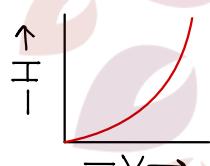

$$V \propto I$$

$$V = IR$$

1. Ohm's Law is not valid for semi-conductor electronic devices like diode & transistor.
2. Ohm's Law is only valid for metallic conductor. Even not valid for metallic conductor at high potential difference.

15. A battery of emf 12V and internal resistance of  $2\ \Omega$  connected to resistor. If 0.5A current flows through circuit then calculate resistance of resistor. If the circuit is closed what will be terminal voltage of cell. [1+1=2]

⇒

$$E = 12V$$

$$\gamma = 2\ \Omega$$

$$I = 0.5A$$

$$R = ?, V = ?$$

$$V = E - IR$$

$$V = 12 - (0.5 \times 2)$$

$$V = 12 - 1$$

$$V = 11V$$

$$V = IR$$

$$R = \frac{V}{I}$$

$$R = \frac{12}{0.5}$$

$$R = 24\ \Omega$$

## BOARD-2018

16. The resistance of a conductor is  $x\Omega$  at  $0^\circ\text{C}$  temp. Find the temp. at which resistance of conductor become  $3x\Omega$ . The temp. coefficient of resistance for conductor is  $0.4 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$  which is constant.

$$\Rightarrow R_1 = x\Omega$$

$$R_2 = 3x\Omega$$

$$T_1 = 0^\circ\text{C}$$

$$T_2 = ?$$

$$\alpha = 0.4 \times 10^{-2} \text{ }^\circ\text{C}^{-1}$$

$$R_2 = R_1 [1 + \alpha (T_2 - T_1)]$$

$$\frac{R_2}{R_1} = 1 + \alpha (T_2 - T_1)$$

$$\frac{3x}{x} = 1 + \alpha (T_2 - T_1)$$

$$2 = \alpha (T_2 - T_1)$$

$$T_2 - T_1 = \frac{2}{0.4 \times 10^{-2}}$$

$$T_2 = 5 \times 10^2 + T_1$$

$$T_2 = 500 + 0^\circ\text{C}$$

$$T_2 = 500^\circ\text{C}$$

17. Wheat stone Bridge.

## BOARD-2018 (Supp)

18. The value of physical quantities  $P$  &  $\varphi$  for a conductor is  $4\Omega$  and  $24 \times 10^{-8} \Omega \text{xm}$ . write new values of  $P$  &  $\varphi$  if length becomes one fourth. [1]

$$\Rightarrow P = 4\Omega \quad \varphi = 24 \times 10^{-8} \Omega \text{xm}$$

↳ Resistance      ↳ Resistivity

if length becomes  $1/4^{\text{th}}$

$$(i) P = 1\Omega \quad (\text{Resistance } [P] \propto \text{length})$$

$$(ii) \varphi = 24 \times 10^{-8} \Omega \text{xm} \quad (\text{Resistivity } (\varphi) \text{ doesn't depend on length}).$$

19. Deduct the microscopic form of ohm's Law [2 Marks]

$V = IR$  (ohm's Law) is often stated in an equivalent form  $J = \sigma E$  where-

$J$  = current density

$\sigma$  = conductivity

$E$  = electric field

vector form:-

$$\vec{J} = \sigma \vec{E}$$

Derivation -

$$V = IR \quad \text{--- (1)}$$

$$\text{Resistivity } \rho = \frac{RA}{l} \quad \text{then } R = \frac{\rho l}{A}$$

Put in eqn (1)

$$V = \frac{I \rho l}{A}$$

$$\frac{V}{l} = \frac{I \rho}{A}$$

$$E = \frac{I \rho}{A} \quad \left\{ \begin{array}{l} \uparrow \text{Electric field} \\ E = \frac{V}{l} \end{array} \right\}$$

$$E = J \rho \quad \left\{ \begin{array}{l} J = I/A \\ \downarrow \text{current density} \end{array} \right\}$$


$$E = J \times \frac{1}{\sigma} \quad \left\{ \begin{array}{l} \sigma = \text{conductivity} \end{array} \right\}$$

$$J = \sigma E$$

$$\text{Or} \quad \vec{J} = \sigma \vec{E}$$

BOARD - 2019

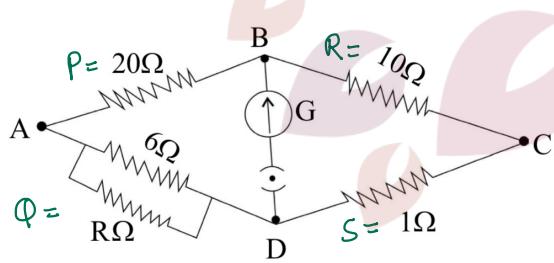20. Find Unknown resistance in balanced state of WSB.



$\Rightarrow$  At Balanced state

$$\frac{P}{R} = \frac{S}{R}$$

$$\frac{20}{R} = \frac{10}{1}$$

$$R = \frac{20}{10} = 2 \Omega$$

$6 \Omega$  &  $R \Omega$  are in parallel and equivalent  
i.e.  $R = 2 \Omega$

$$\frac{1}{6} + \frac{1}{R} = \frac{1}{2}$$

$$\frac{1}{R} = \frac{1}{2} - \frac{1}{6}$$

$$\frac{1}{R} = \frac{3-1}{6}$$


$$R = 6/2 = 3 \Omega \quad \text{Ans.}$$

BOARD - 2020

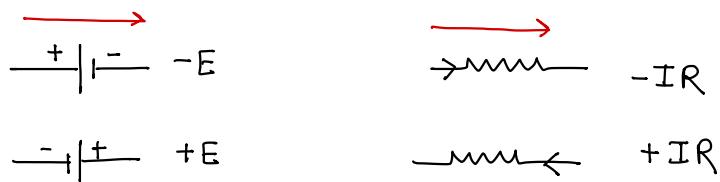21. Write Kirchoff's Second Rule.

- $\Rightarrow$  Also Known as Loop Law / Mesh Law
- $\Rightarrow$  Algebraic sum of all the voltage in any loop is always zero.
- $\Rightarrow$  Only valid for closed circuit

→ Based on Law of conservation of Energy.



### BOARD-2020 (Supp)

22. Define current density. [1]  
 23. The length of wire is 1.5m and its cross-section area is  $6 \times 10^{-7} \text{ m}^2$ . If the potential difference at its end is 0.9V. Calculate the current flowing in it. [ $\rho = 5.6 \times 10^{-8} \Omega \text{ m}$ ] [2]

$$\Rightarrow l = 1.5 \text{ m} \quad A = 6 \times 10^{-7} \text{ m}^2$$

$$V = 0.9 \text{ V} \quad I = ?$$

$$\rho = 5.6 \times 10^{-8} \Omega \text{ m}$$

$$V = IR$$

$$I = \frac{V}{R} = \frac{0.9}{14 \times 10^{-7}}$$

$$I = \frac{90}{14} = 6.42 \text{ A}$$

$$R = \frac{\rho l}{A}$$

$$R = \frac{5.6 \times 10^{-8} \times 1.5}{6 \times 10^{-7}}$$

$$R = 1.4 \times 10^1 \Omega$$

### BOARD-2021

24. Unit of electromotive force.

⇒ Volt.

25. Define internal resistance of cell.

⇒ Resistance offered by electrolyte solution in flow of current in cell is called Internal resistance of cell.  
 SI unit =  $\Omega$

26. Draw a Labelled diagram of wsb and obtain condition of balanced point by Kirchoff's Rule.

### BOARD-2022

27. If two cells of emf  $E_1$  &  $E_2$  and internal resistance  $r_1$  &  $r_2$  are in parallel combination. find formula of equivalent emf.

$$\Rightarrow E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$$

28. If 12 resistors of  $1\Omega$  resistance are joined in a cubical network, then calculate the equivalent resistance at corner opposite to diagonals of this network.


BOARD-2023

29. On increasing the temperature, the resistivity of semiconductor   
  $\Rightarrow$  Decreases.

30. Draw a Labelled diagram of wSB and obtain condition of balanced point by Kirchoff's Rule.

BOARD-2024

31. The SI Unit of Resistivity-  
  $\Rightarrow \Omega \times m$

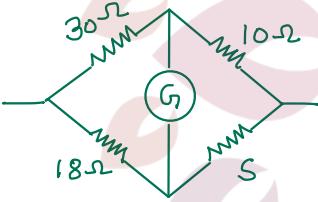
32.   $\Rightarrow$  find S.

$$\frac{30}{18} = \frac{10}{S}$$

$$S = \frac{10 \times 18}{30}$$

$$S = 6\Omega$$

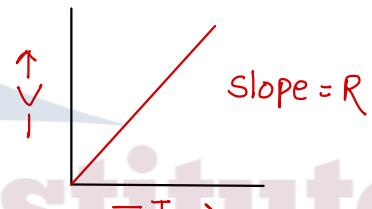33. Draw VI Graph for ohm's Law.  
  $\Rightarrow$



34. Define electromotive force.

Potential difference across the terminal of cell when no current is drawn from the cell.

SI Unit  $\Rightarrow$  volt



LIKE  
SUBSCRIBE  
SHARE

Best of Luck for Exam